

ELECENG 2EI4

Design Project 2 - Voltage Controlled Switch

Instructor: Dr.Haddara
Suchir Ladda - laddas - 400517569
Date: 3/2/2025

As a future member of the engineering profession, the student is responsible for performing the required work in an honest manner, without plagiarism and cheating. Submitting this work with my name and student number is a statement and understanding that this work is my own and adheres to the Academic Integrity Policy of McMaster University and the Code of Conduct of the Professional Engineers of Ontario. Submitted by [**Suchir Ladda, laddas, 400517569**]

Ideal Switches

An ideal switch is a concept of a device that provides electrical conduction with no loss of energy in the ON position and acts as a perfect insulator in the OFF position. While in the ON position, the switch can be imagined to have infinite conduction in such a way that it can dissipate energy without any loss, allowing both input and output voltages to be equal. This results in total energy and power loss, meaning the switch consumes no power. However, in real life applications, actual switches do have some level of resistance but it is quite negligible resulting in very small voltage drops and considerably less loss of energy.

While in the OFF position, the device serves as a perfect insulator and hence can be imagined to have infinite resistance, which eradicates the flow of any form of current through it, thus providing total separation between its terminals. In comparison to an ideal switch, which does not allow any form of leakage current, practical switches do show indications of having low leakage due to errors in the construction material. Although engineers attempt to correct these faults, eradicating them altogether is impossible.

Another key property of an ideal switch is its ability to handle any voltage across its terminals without failure. Whether dealing with millivolts or thousands of volts, the switch remains operational without breakdown. In reality, physical switches have voltage limits, beyond which insulation breakdown, arcing, or material damage can occur, making careful voltage rating considerations necessary in circuit design.

Additionally, an ideal switch allows current to flow equally well in both directions. This bidirectional nature makes it particularly useful in AC circuits or applications where current direction may change frequently. In contrast, many real-world switches, especially semiconductor-based ones, may have a preferred conduction direction or exhibit varying resistances depending on the flow of current.

Non-Idealities

There are many differences between real and ideal switches. One of the key non-idealities is leakage current (I_{off}) when the switch is OFF. Ideally, an open switch should have infinite resistance, preventing any current flow. However, due to material imperfections, stray capacitance, or semiconductor effects, a small leakage current still flows. While typically in the nanoampere range, this can become problematic in low-power applications, causing unintended power consumption or signal integrity issues. Engineers aim to minimize leakage to improve switch isolation.

When the switch is ON, its ON resistance (R_{on}) is another major non-ideality. Unlike an ideal switch, which would have zero resistance, real switches always exhibit some small resistance, leading to a voltage drop across the switch. This drop is given by $V_{switch} = I \times R_{on}$, meaning the output voltage is slightly lower than the input. Additionally, power dissipation occurs as $P = I^2 \times R_{on}$, which generates heat and reduces efficiency. Lowering

R_{on} is crucial in power electronics and signal applications to minimize losses and maximize performance.

Real switches are also constrained by a limited voltage range, meaning they can only operate safely between a minimum (V_{min}) and a maximum (V_{max}) voltage. If the applied voltage exceeds V_{max} , the switch may experience insulation breakdown, arcing, or complete failure. Conversely, if the voltage is below V_{min} , the switch may not activate properly, particularly in semiconductor-based switches that require a minimum gate voltage to turn on. Unlike an ideal switch, which would function across all voltage levels, real switches must operate within defined voltage limits.

Lastly, the bidirectionality of a real switch is often imperfect. Ideally, the ON resistance (R_{on}) should remain constant regardless of whether current flows in one direction ($V_1 > V_2$) or the other ($V_1 < V_2$). However, in many real switches, particularly semiconductor devices like MOSFETs and BJTs, resistance can vary based on voltage polarity and direction. Some switches are optimized for a single direction, making them less suitable for AC or bidirectional applications. A truly bidirectional switch would maintain a consistent resistance regardless of current direction.

Test Plan

To accurately quantify the non-idealities of a real switch, we will conduct experiments for each key deviation from ideal behavior. The test setup will involve a controlled power supply, measurement instruments such as oscilloscopes and multimeters, and various input signals to evaluate the switch's performance under different conditions.

Switch 1 Test Plan

The first test will measure the ON-state resistance (R_{on}) and voltage drop, which determine how much resistance the switch introduces when conducting. To do this, we will set $V_{control}$ to 0V to turn the switch ON, apply V_{supply} at 5V, and set V_1 to 5V while connecting V_2 to a load. By measuring the voltages at V_1 and V_2 while the switch is conducting, along with the current flowing through the switch, we can calculate R_{on} using the formula $R_{on} = (V_1 - V_2) / I$. Additionally, power dissipation due to the switch resistance can be determined using $P = I^2 \times R_{on}$. If R_{on} is too high, it can lead to unwanted voltage drops and excessive power dissipation, making the switch inefficient in high-current applications.

Another important test will evaluate the voltage operating range (V_{min} and V_{max}), which determines the range of voltages the switch can handle before it stops functioning as expected. In this test, V_{supply} will be gradually increased from 0V to 10V while keeping $V_{control} = 0V$ to observe the switch's behavior at both low and high voltages. We will monitor the voltage at V_2 and identify at what point the switch no longer operates correctly. This will allow us to determine V_{min} , the minimum voltage required for the switch to

function, and V_{max} , the maximum voltage beyond which failure occurs due to insulation breakdown or excessive leakage current.

Finally, we will test bidirectional conductance by checking whether the switch behaves the same regardless of current direction. To do this, we will set $V_{control}$ to 0V to turn the switch ON, apply V_{supply} at 5V, and measure the ON resistance when $V_1 > V_2$. We will then reverse the voltage polarity so that $V_2 > V_1$ and measure the resistance again. If R_{on} varies significantly between these two cases, it indicates that the switch is not truly bidirectional and may introduce inconsistencies in AC or bidirectional circuits.

Switch 2 Test Plan

When the switch is turned ON, it introduces a small but measurable resistance that affects performance. To measure this, $V_{control}$ will be set to 0V to close the switch. A voltage of 5V will be applied to V_1 , and we will alternate between connecting V_A and V_B to observe the switching behavior. By measuring the voltage difference between V_1 and V_A (or V_B) while recording the current flow, the ON resistance can be calculated as $R_{on} = (V_1 - V_A) / I$. If R_{on} is too high, it will cause excessive voltage drop and power dissipation, which is undesirable in high-current applications.

The switch should operate correctly over a defined voltage range. To test this, V_{supply} will be ramped from 0V to 10V, while $V_{control}$ remains at 0V. The voltages at V_1 , V_A , and V_B will be monitored to determine if the switch continues to function correctly throughout the range. If the switch starts behaving unpredictably outside a certain voltage range, we can define V_{min} and V_{max} , indicating the limits within which the switch performs as expected.

This test determines whether the switch behaves identically regardless of the direction of current flow. With $V_{control}$ set to 0V, a voltage will be applied first at V_1 and then at V_A while keeping V_B at ground. The resistance will be measured in both configurations to ensure that the switch provides consistent conduction in both directions. If significant variations are observed, it suggests that the switch is not fully bidirectional and may introduce performance inconsistencies in AC applications.

By conducting these tests, we can quantify the non-idealities of Switch Type 2 and determine whether it meets the necessary performance criteria.

Switch type 1

Circuit Schematic

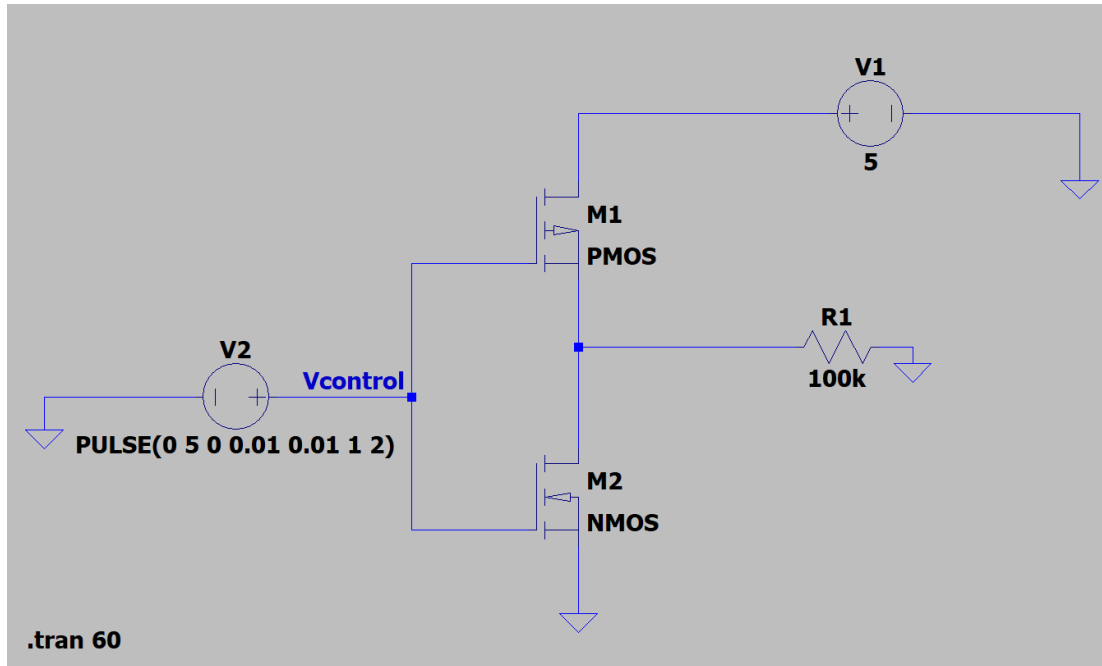


Figure 1: Circuit Schematic of Switch 1

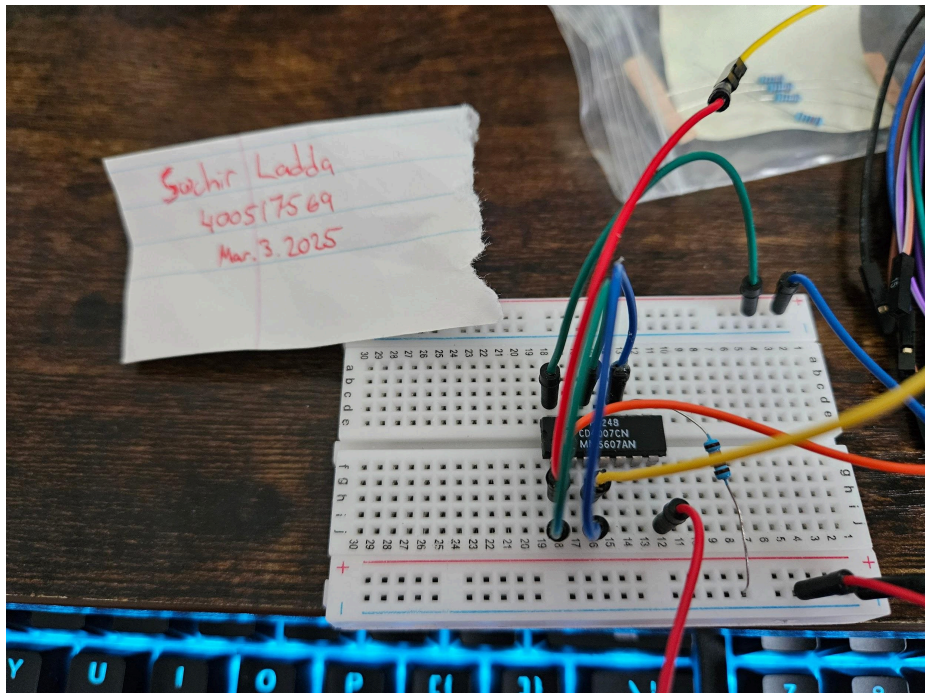


Figure 2: Physical Circuit Implementation of Switch 1

Measurements

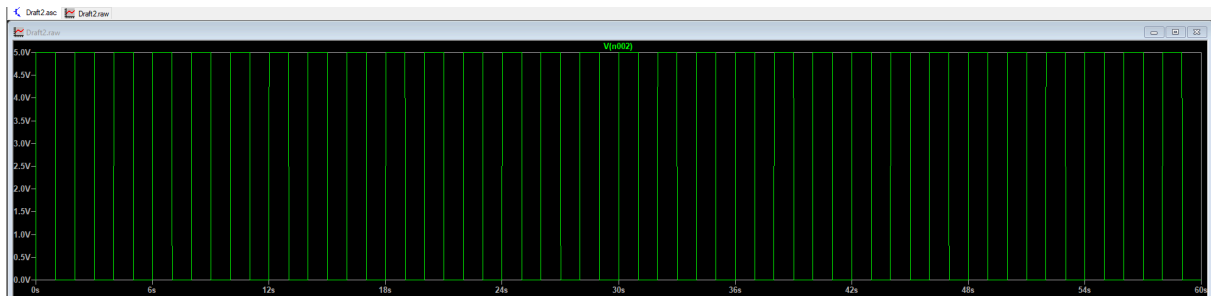


Figure 3: Square wave pulse from 0-5V being sent in

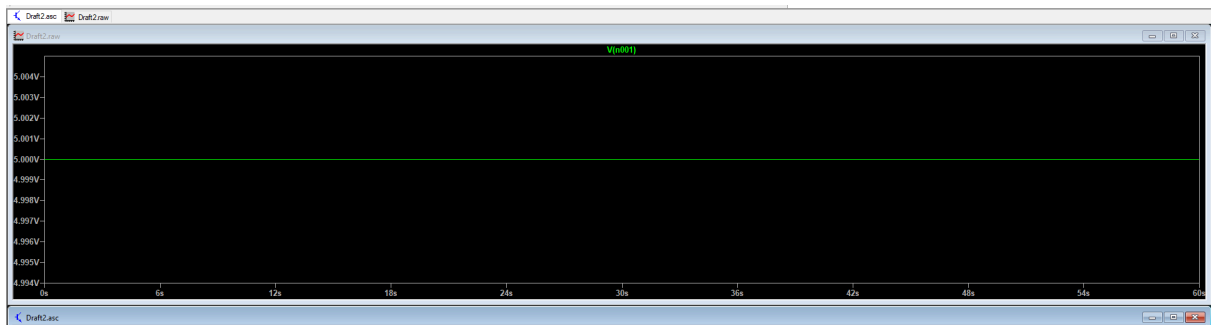


Figure 4: 5V DC input

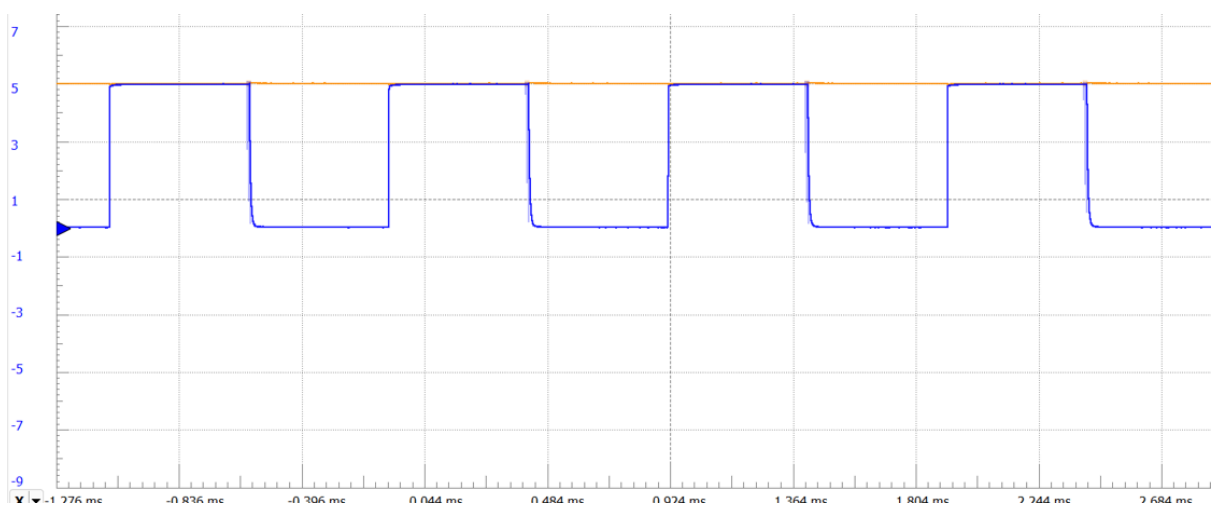


Figure 5: AD3 output

Theoretical Explanation

The switch design is bidirectional, incorporating both n-type and p-type MOSFETs. Bidirectionality is a key characteristic of an ideal switch, making it an essential factor in this design. The final output screenshot illustrates the switch's behavior, where the control voltage ($V_{control}$) alternates between 0V and 5V. When $V_{control}$ is 5V, the switch is in the OFF state and should exhibit the property that $I_1=I_2=0$. Conversely, when $V_{control}$ is 0V, the switch enters the ON state, ensuring that $V_1=V_2$.

To verify these theoretical predictions, we analyzed the final output. When $V_{control}$ is 0V, V_2 measures 5V, confirming that $V_1=V_2$ as expected. Additionally, a 100k Ω resistor was added to the output of the switch. However, when $V_{control}$ is set to 5V, V_2 drops to 0V, regardless of V_1 being 5V, demonstrating the expected OFF-state behavior.

These observations can also be confirmed mathematically. In the ON state, the resistance is calculated as:

$$R_{ON} = \frac{5V - 5V}{50\mu A} = 0\Omega$$

Similarly, in the OFF state, the resistance is given by:

$$R_{OFF} = \frac{0V - 5V}{15nA} = \infty\Omega$$

Design Tradeoffs

The major tradeoff in this design was balancing the need to demonstrate all required aspects while working within the limitations of available components. The simplest design considered used only a single MOSFET, but it was not bidirectionally conductive and was therefore not selected as the final design. On the other hand, more complex circuits involved three or four MOSFETs and additional components like inverters, which were not permitted in the circuit's construction. To strike a balance between complexity and simplicity while accurately representing the key characteristics of an ideal switch, the chosen design was selected.

Switch type 2

Circuit Schematic

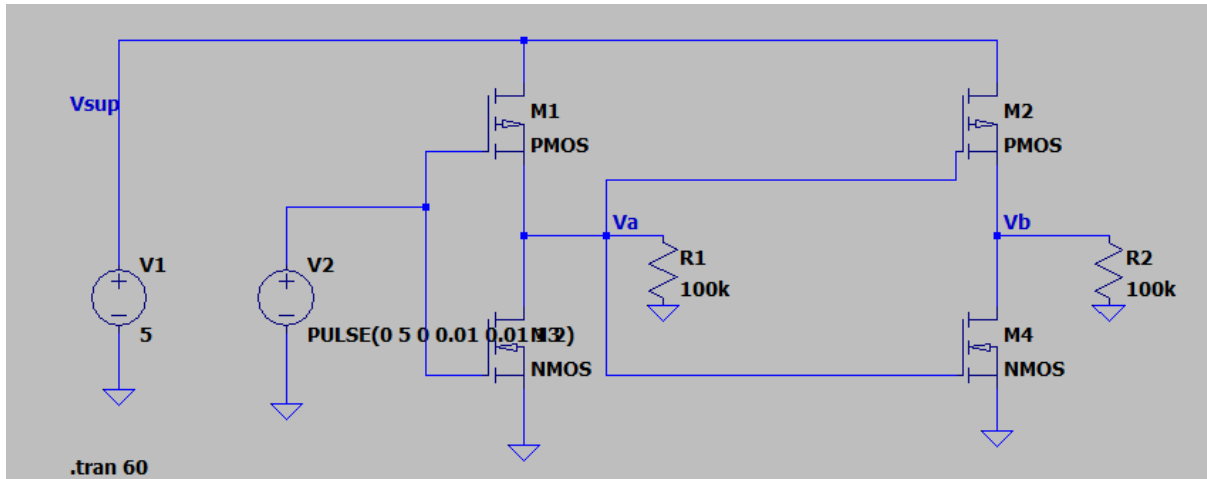


Figure 6: Circuit Schematic of Switch 2

Measurements

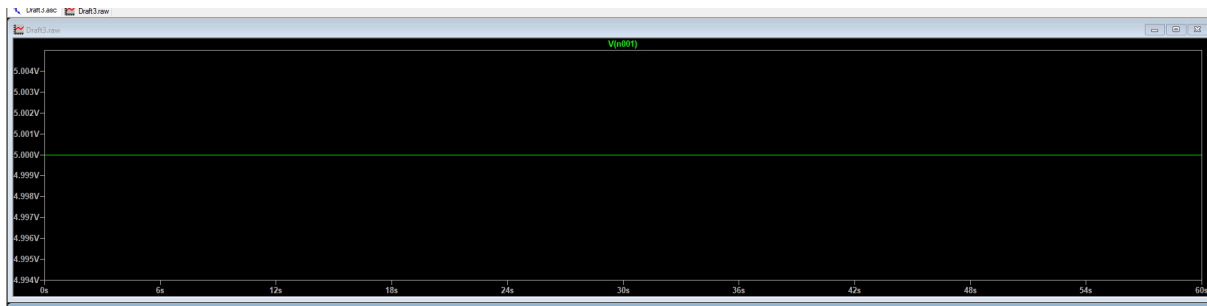


Figure 7: 5V input

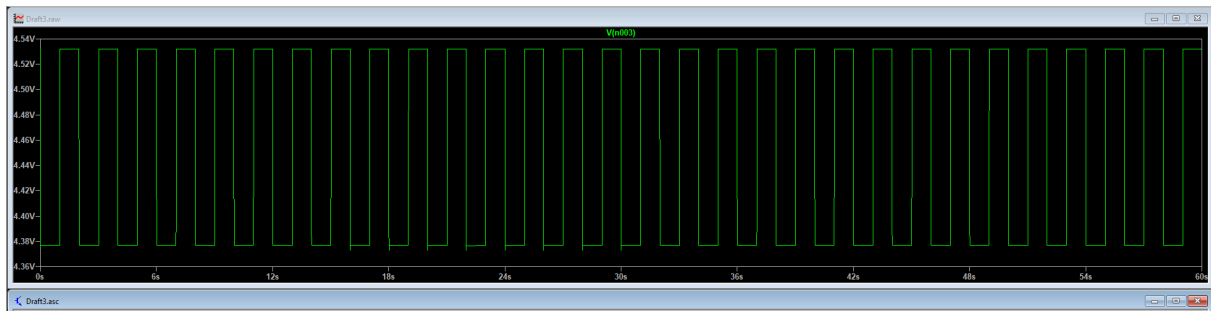


Figure 8: V_a output

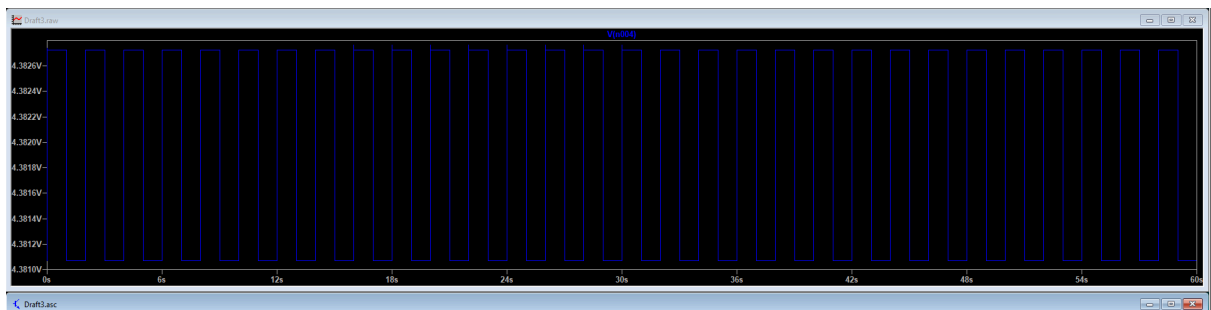


Figure 9: V_b output

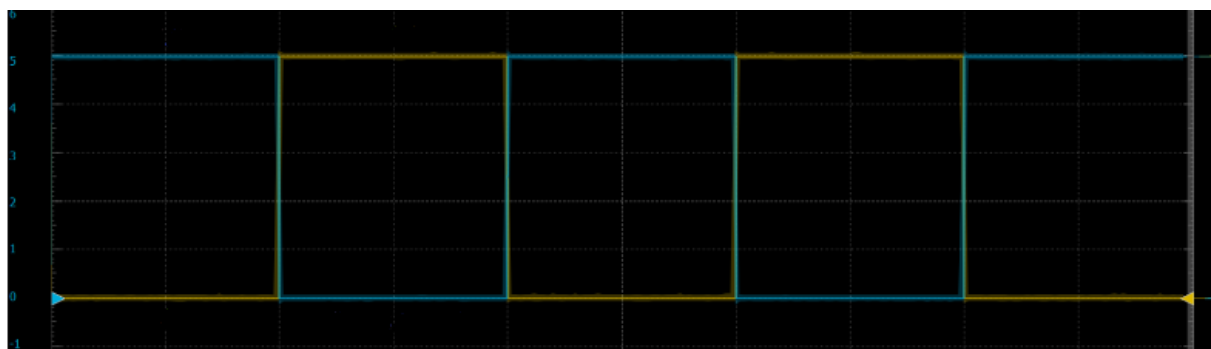


Figure 10: $AD3$ output

Theoretical Explanation

The above results depict the simulation output for the Switch Type 2 design. To evaluate the switch's functionality, the voltages V_a , V_b , and the circuit's current were analyzed to determine the switch's output behavior under different control voltage conditions.

Specifically, when V_{control} is set to 0V, the circuit's output should be taken from V_a , and when V_{control} is 5V, the output should correspond to V_b .

By examining the provided graphs, we can confirm this expected behavior. When V_{control} is at 5V, V_b measures 5V, while V_a is 0V. Conversely, when V_{control} is 0V, V_a registers 5V, and V_b drops to 0V. These results indicate that the circuit is operating correctly.

Design Tradeoffs

Several trade-offs were considered in the construction of the second switch design, with the primary decision revolving around balancing complexity and practicality. The most significant compromise was opting for a slightly less comprehensive design in favor of simplicity and ease of implementation.

An alternative approach involved a more intricate configuration using both MOSFET ICs provided in the 2EI4. This design closely resembled an ideal switch, offering better performance in terms of bidirectional conduction and minimal resistance. However, due to the increased complexity, both in terms of circuit design and physical implementation, a more streamlined solution was chosen.

References

- [1] A. S. Sedra, K. C. Smith, T. C. Carusone, and V. Gaudet, Microelectronic circuits, 8th ed.
New York, NY: Oxford University Press, 2019.